 


## Quiz Problems (50 points total)

### Problem 1 (12 points)

Answer the questions on the following gate network.



1. (6 points) Given the following timing parameters, calculate the setup time, hold time and propagation delay of the sequential network. All inverted inputs are available and there are no additional NOT gates.

JK flip-flop characteristics:  $t_{su}(\text{cell}) = 0.8 \text{ ns}$ ,  $t_h(\text{cell}) = 2.7 \text{ ns}$ ,  $t_p(\text{cell}) = 1.8 \text{ ns}$

Gate characteristics:  $t_p(\text{AND2}) = t_p(\text{OR2}) = 3.5 \text{ ns}$ ,  $t_p(\text{AND3}) = 4.0 \text{ ns}$

**Solution** For  $d1^x$ , the worst case path is through the J input for  $y_0$ , where the signal needs to go through two gate levels. The logic for the output is just an AND gate.

$$\begin{aligned} d1^x &= t_p(\text{AND2}) + t_p(\text{OR2}) = 3.5 + 3.5 = 7.0(\text{ns}) \\ d2 &= t_p(\text{AND2}) = 3.5(\text{ns}) \end{aligned}$$

Now using this we can calculate the following.

Network setup time:

$$\begin{aligned} t_{su}(\text{net}) &= d1^x + t_{su}(\text{cell}) \\ &= 7.0 + 0.8 \\ &= 7.8 \text{ (ns)} \end{aligned}$$

Network hold time  $t_h(\text{net}) = t_h(\text{cell}) = 2.7 \text{ (ns)}$

Network propagation delay

$$\begin{aligned} t_p(\text{net}) &= t_p(\text{cell}) + d2 \\ &= 1.8 + 3.5 = 5.3 \text{ (ns)} \end{aligned}$$

2. **(6 points)**  $t_{in} = 2.5 \text{ ns}$  and  $t_{out} = 1.5 \text{ ns}$ . Calculate  $T_x$ ,  $T_y$  and  $T_z$  values for this system.

**Solution** For  $d1^y$ , the worst case path is through the 3-input AND gate at the K input for  $y_1$ . Therefore,

$$d1^y = t_p(\text{AND3}) = 4.0(\text{ns})$$

With this and numbers from the previous part, we can write:

$$\begin{aligned} T_x &= t_{in} + d1^x + t_{su}(\text{cell}) = 2.5 + 7.0 + 0.8 = 10.3 \text{ (ns)} \\ T_y &= t_p(\text{cell}) + d1^y + t_{su}(\text{cell}) = 1.8 + 4.0 + 0.8 = 6.6 \text{ (ns)} \\ T_z &= t_p(\text{cell}) + d2 + t_{out} = 1.8 + 3.5 + 1.5 = 6.8 \text{ (ns)} \end{aligned}$$

## Problem 2 (8 points)

We wish to create an SR flip-flop using a T flip-flop. The transition table for the SR flip-flop is:

$PS = Q(t)$	$S(t)R(t)$			
	00	01	10	11
0	0	0	1	-
1	1	0	1	-
$NS = Q(t+1)$				

1. **(3 points)** Fill in the table below.

**Solution** From the given transition table, we can write:

$PS = Q(t)$	$S(t)R(t)$				$S(t)R(t)$			
	00	01	10	11	00	01	10	11
0	0	0	1	-	0	0	1	-
1	1	0	1	-	0	1	0	-
$NS = Q(t+1)$					$T$			


2. **(5 points)** Using the table, obtain the expression for  $T$  and draw the final circuit.

**Solution** From the completed table, we can get the following K-map:

		R	
Q	0	0	-
	0	1	-
		S	

and from this we get  $T = QR + Q'S$ .

The final circuit looks like:

 


### Problem 3 (30 points)

Design a modulo-3 counter using JK flip-flops. Use a Moore machine. The counter specifications are as shown here:

Input:  $x(t) \in \{0, 1\}$   
Output:  $z(t) \in \{0, 1, 2\}$   
State:  $s(t) \in \{S_0, S_1, S_2\}$   
Initial state:  $s(0) = S_0$   
Function: In modulo-3, the system counts the number of 1's in the input sequence  $x(0, t-1)$

- (6 points) Draw the state transition diagram for the counter. Clearly show **ALL** transitions from each state. Show the output of each state.

 **Solution** The state transition diagram is shown.



- (8 points) Using the following **unconventional** encoding for the states, complete the table below.


	$Q_1$	$Q_0$
$S_0$	0	0
$S_1$	1	1
$S_2$	0	1

**Solution**

$Q_1Q_0$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
00	00	11	0- 0-	1- 1-
01	01	00	0- -0	0- -1
10	--	--	-- --	-- --
11	11	01	-0 -0	-1 -0
	$NS$		$J_1K_1J_0K_0$	

- (12 points) Complete the K-maps and obtain the minimal expressions for  $J_1$ ,  $K_1$ ,  $J_0$  and  $K_0$ .

**Solution**

 

From these we get:

$$\begin{aligned}
 J_1 &= Q_0'x \\
 K_1 &= x \\
 J_0 &= x \\
 K_0 &= Q_1'x
 \end{aligned}$$

4. (4 points) The output is encoded using conventional binary numbers as shown.

	$z_1$	$z_0$
0	0	0
1	0	1
2	1	0

Obtain the expressions for the output bits  $z_1$  and  $z_0$ . Since this is a Moore machine, show them in terms of the state bits  $Q_1$  and  $Q_0$ . If possible, try to obtain the simplest expression by utilizing don't-cares.

**Solution** From the state encoding and output bit encoding, we can get:

$Q_1$	$Q_0$	State	Output value	$z_1$	$z_0$
0	0	$S_0$	0	0	0
0	1	$S_2$	2	1	0
1	0	—	—	—	—
1	1	$S_1$	1	0	1

From here, we can write  $z_1 = Q_1'Q_0$  and  $z_0 = Q_1$ .