

# [CS M51A FALL 18] CH5-SAMPLE-HOMEWORK

## Practice Exercises

From the book: 5.5, 5.7, 5.15. Solutions are posted.

---

## Homework Problems

### Problem 1 (20 points)

For  $f(x, y, z, w) = \prod M(1, 8, 9, 12)$

1. Using K-maps, find all the prime implicants.
2. Which of these prime implicants are essential?
3. Write the minimal sum of products for  $f$ .
4. Find all the prime implicants.
5. Which of these prime implicants are essential?
6. Write the minimal product of sums for  $f$ .

### Problem 2 (10 points)

We would like to examine how K-maps can be used to obtain minimal sum-of-product expressions. We are given the following expression.

$$E(x, y, z, w) = xy' + xzw + yw$$

1. Using the given expression, fill in the table below.

$x$	$y$	$z$	$w$	$E$
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

2. Draw the K-map for the table.

3. Identify the essential prime implicants. Is  $xzw$  essential? Why or why not?

### Problem 3 (20 points)

We are given a module with four input bits,  $x_1, x_0, y_1, y_0$  and three output bits,  $z_2, z_1, z_0$ , which are:

$$z_2 = \sum m(7, 10, 11, 13, 14, 15)$$

$$z_1 = \sum m(2, 3, 5, 6, 8, 9, 12, 15)$$

$$z_0 = \sum m(1, 3, 4, 6, 9, 11, 12, 14)$$

1. Fill in the table.

$x_1$	$x_0$	$y_1$	$y_0$	$z_2$	$z_1$	$z_0$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

2. Draw K-maps for each output bit. Find the prime implicants.

3. Write the minimal sum of products expression for each  $z$  bit.
4. Looking back at the table, can you identify the high-level function of the module?

#### Problem 4 (20 points)

We would like to design a BCD-to-Gray-Code converter. The Gray Code is a coding scheme where each number sequence differs from its predecessor by exactly one bit. The Gray code for decimal digits is shown in the following table.

Coded value	$z_3$	$z_2$	$z_1$	$z_0$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	1
3	0	0	1	0
4	0	1	1	0
5	1	1	1	0
6	1	0	1	0
7	1	0	1	1
8	1	0	0	1
9	1	0	0	0

1. Write the truth table for the converter. How many input bits do we need? Do not forget don't-care cases.
2. Draw the K-maps for each  $z$  bit. Find the prime implicants.
3. Write the minimal sum of products for each  $z$  bit. How many gates would we need for an AND-OR network implementation? Assume that the complements of the inputs are available.