


[CS M51A] SOLUTION TO SAMPLE CHAPTER 5 HMW

Problem 1 (20 points)

For $f(x, y, z, w) = \prod M(1, 8, 9, 12)$

- Using K-maps, find all the prime implicants.

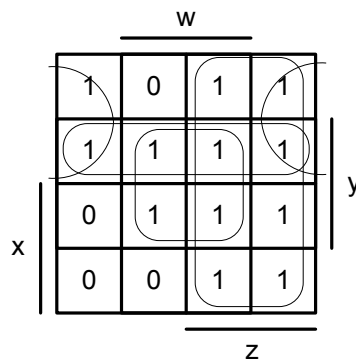Solution The prime implicants are shown in the K-map.



The equivalent product terms are z , yw , $x'w'$ and $x'y$.

- Which of these prime implicants are essential?

Solution $x'y$ does not have any squares that it covers alone, therefore it is not essential.

- Write the minimal sum of products for f .

Solution Excluding the non-essential prime, we get $z + yw + x'w'$.

- Find all the prime implicants.

Solution

		w				
		1	0	1	1	
		1	1	1	1	
		0	1	1	1	
		0	0	1	1	
		z				
	x					y

The equivalent sum terms are $(x' + z + w)$, $(y + z + w')$ and $(x' + y + z)$.

5. Which of these prime implicants are essential?

Solution $(x' + y + z)$ does not have any squares that it covers alone, therefore it is not essential.

6. Write the minimal product of sums for f .

Solution Excluding the non-essential prime, we get $(x' + z + w)(y + z + w')$.

Problem 2 (10 points)

We would like to examine how K-maps can be used to obtain minimal sum-of-product expressions. We are given the following expression.

$$E(x, y, z, w) = xy' + xzw + yw$$

1. Using the given expression, fill in the table below.

Solution

x	y	z	w	E
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

2. Draw the K-map for the table.

Solution The K-map is shown here.

		w				
		0	0	0	0	
		0	1	1	0	
		0	1	1	0	y
x		1	1	1	1	
		z				

3. Identify the essential prime implicants. Is xzw essential? Why or why not?

Solution From the above K-map, we can see that the two essential prime implicants are xy' and yw . xzw covers two squares, and since each one is also covered by the two prime implicants, it is not essential.

Problem 3 (20 points)

We are given a module with four input bits, x_1, x_0, y_1, y_0 and three output bits, z_2, z_1, z_0 , which are:

$$\begin{aligned} z_2 &= \sum m(7, 10, 11, 13, 14, 15) \\ z_1 &= \sum m(2, 3, 5, 6, 8, 9, 12, 15) \\ z_0 &= \sum m(1, 3, 4, 6, 9, 11, 12, 14) \end{aligned}$$

1. Fill in the table.

Solution

x_1	x_0	y_1	y_0	z_2	z_1	z_0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

2. Draw K-maps for each output bit. Find the prime implicants.

Solution The input bits are x_1, x_0, y_1, y_0 with x_1 being the most significant bit. The K-maps for each bit is as shown below.

Prime implicants for z_2 : x_1y_1 , $x_1x_0y_0$, $x_0y_1y_0$

		y_0				
		0	0	0	0	
		0	0	1	0	x_0
x_1		0	1	1	1	
		0	0	1	1	
		y_1				

Prime implicants for z_1 : $x_1y'_1y'_0$, $x_1x'_0y'_1$, $x'_1x_0y'_1y_0$, $x_1x_0y_1y_0$, $x'_1x'_0y_1$, $x'_1y_1y'_0$

		y_0			
		0	0	1	1
		0	1	0	1
x_1		1	0	1	0
		1	1	0	0
		y_1			
				x_0	

Prime implicants for z_0 : $x_0y'_0$, x'_0y_0

		y_0				
		0	1	1	0	
		1	0	0	1	x_0
x_1		1	0	0	1	
		0	1	1	0	
		y_1				

3. Write the minimal sum of products expression for each z bit.

Solution All prime implicants for the outputs are essential here. Therefore the minimal SoPs are:

$$\begin{aligned}
 z_2 &= x_1y_1 + x_1x_0y_0 + x_0y_1y_0 \\
 z_1 &= x_1y'_1y'_0 + x_1x'_0y'_1 + x'_1x_0y'_1y_0 + x_1x_0y_1y_0 + x'_1x'_0y_1 + x'_1y_1y'_0 \\
 z_0 &= x_0y'_0 + x'_0y_0
 \end{aligned}$$

4. Looking back at the table, can you identify the high-level function of the module?

Solution Looking at the inputs as separate binary values of x and y , we can see that the resulting z is a sum of x and y . The module is an adder which adds the two inputs x and y .

Problem 4 (20 points)

We would like to design a BCD-to-Gray-Code converter. The Gray Code is a coding scheme where each number sequence differs from its predecessor by exactly one bit. The variation we use for this problem is for encoding a decimal digit. The actual code values used in this problem are shown in the table below.

Coded value	z_3	z_2	z_1	z_0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	1
3	0	0	1	0
4	0	1	1	0
5	1	1	1	0
6	1	0	1	0
7	1	0	1	1
8	1	0	0	1
9	1	0	0	0

1. Write the truth table for the converter. How many input bits do we need? Do not forget don't-care cases.

Solution To accomodate for digits from 0 to 9, we need four binary bits, which we will label x_3 down to x_0 . The truth table is as shown:

x_3	x_2	x_1	x_0	z_3	z_2	z_1	z_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	0	-	-	-	-
1	0	1	1	-	-	-	-
1	1	0	0	-	-	-	-
1	1	0	1	-	-	-	-
1	1	1	0	-	-	-	-
1	1	1	1	-	-	-	-

2. Draw the K-maps for each z bit. Find the prime implicants.

Solution Prime implicants for z_3 : x_3 , x_2x_0 , x_2x_1

	x_0				
	0	0	0	0	
	0	1	1	1	x_2
x_3	-	-	-	-	
	1	1	-	-	
	x_1				

Prime implicants for z_2 : $x_2x'_1$

	x_0				
	0	0	0	0	
	1	1	0	0	x_2
x_3	-	-	-	-	
	0	0	-	-	
	x_1				

Prime implicants for z_1 : x_2, x_1

	x_0				
	0	0	1	1	
	1	1	1	1	x_2
x_3	-	-	-	-	
	0	0	-	-	
	x_1				

Prime implicants for z_0 : $x'_3x'_2x'_1x_0, x_3x'_0, x_2x_1x_0, x'_2x_1x'_0$

		x_0				
		0	1	0	1	
		0	0	1	0	
		-	-	-	-	x_2
x_3		1	0	-	-	
		x_1				

3. Write the minimal sum of products for each z bit. How many gates would we need for an AND-OR network implementation?

Solution

$$z_3 = x_3 + x_2x_0 + x_2x_1$$

$$z_2 = x_2x'_1$$

$$z_1 = x_2 + x_1$$

$$z_0 = x'_3x'_2x'_1x_0 + x_3x'_0 + x_2x_1x_0 + x'_2x_1x'_0$$

Assuming that the inverse of the input is available, the total number of gates needed is:

z_3 : 1 OR3, 2 AND2

z_2 : 1 AND2

z_1 : 1 OR2

z_0 : 1 OR4, 1 AND4, 2 AND3, 1 AND2

Total: 10 gates

