


[CS M51A FALL 18] SOLUTION TO HOMEWORK 3

Due: 10/26/18

Homework Problems (80 points total)

 Problem 1 (10 Points)

Show that the network in the figure below is combinational even though there is a physical loop.



Solution

$z_1' = \text{value of } z_1 \text{ at a prev. point}$

$$z_0 = z_1' \bar{b} + be + c$$

$$z_1 = (a\bar{b} + bz_0) d$$

Replacing z_0 in z_1

$$z_1 = [a\bar{b} + b(z_1' \bar{b} + be + c)] d$$

$$z_1 = [a\bar{b} + (\bar{b} z_1' + be + bc)] d$$

$$z_1 = [a\bar{b} + \cancel{z_1'} + be + bc] d$$

Hence z_1 does not depend on previous value of itself (or any other previous)

Hence, combinational


[\because b interrupts the loop basically]

Problem 2 (10 points)

For the following tabular description of a network, give its graphical description and determine whether the network is valid. If not valid, make modifications on the description so that it is valid.

From	To	Gate	Type	Input	Output
R	A ₁	A	AND2	A ₁	A
S	A ₂			A ₂	
A	B ₁	B	NOT	B ₁	B
A ₂	C ₁	C	AND3	C ₁	C
T	C ₂			C ₂	
X	C ₃			C ₃	
C	D ₁	D	OR2	D ₁	D
Y	D ₂			D ₂	
B	E ₁	E	OR2	E ₁	E
D	E ₂			E ₂	
E	Z				

Solution

 

The network is valid.

Problem 3 (10 points)

Show that the set {XNOR,OR} is universal. You can use constant 0 or 1 (only one of them).

Solution

If we show that NOT can be realized, then since {OR,NOT} is universal, we can say that {XNOR,OR} is universal.


$$XNOR(x, y) = xy + x'y'$$

Since we can use the constant 0, it is clear that:


$$NOT(x) = XNOR(x, 0) = x.0 + x'.1 = x'$$

Problem 4 (10 points)

 1. Analyze the NAND-NOR network shown in the figure below. Obtain switching expressions for the outputs.



Solution

 

$$\begin{aligned}
 z_0 &= (T_3 + T_4)' \\
 &= ((x_0 T_1)' + (T_1 + x_0)')' \\
 &= (x_0' + T_1' + T_1' x_0')' \\
 &= (x_0' + T_1')' \\
 &= (x_0' + ((x_0 x_1)'))' \\
 &= (x_0' + x_0 x_1)' \\
 &= x_0 (x_0' + x_1') \\
 &= x_0 x_1'
 \end{aligned}$$


$$\begin{aligned}
Z_1 &= (T_2 T_3)' \\
&= ((x_1 T_1)' (T_1 x_0)')' \\
&= x_1 T_1 + x_0 \bar{T}_1 \\
&= (x_0 x_1)' (x_0 + x_1) \\
&= (x_0' + x_1') (x_0 + x_1) \\
&= x_0' x_1 + x_1' x_0 \\
&= x_0 \oplus x_1
\end{aligned}$$

Can be done using mixed logic also. Will be simpler that way.

 Problem 5 (40 points)

Analyze the network as shown in the figure below. Obtain:

- Switching expressions for each of the outputs.
- A high-level description assuming that the bit-vector $\underline{s} = (s_2, s_1, s_0)$ represents an integer in the radix-2 representation.
- For the gate characteristics given in Table 4.1, determine (decompose the gates not available in the table):
 - the load factor of each input;
 - the load for each gate output; and
 - the delay of the network. Give this delay in terms of the load of the output.
- Give a timing diagram showing the delays in the critical path.



Solution a. The switching expression for output z is:

$$z = E(I_0 s'_2 s'_1 s'_0 + I_1 s'_2 s'_1 s_0 + I_2 s'_2 s_1 s'_0 + I_3 s'_2 s_1 s_0 + I_4 s_2 s'_1 s'_0 + I_5 s_2 s'_1 s_0 + I_6 s_2 s_1 s'_0 + I_7 s_2 s_1 s_0)$$

b. If n is the decimal representation of $\{s_2, s_1, s_0\}$, then : If $E = 1$, $z = I_n$
Else 0.

It is kind of like a 8 X 1 selector.

c. The load factor of each input is 1, since each input is connected to only one gate input.

Load for NOT connected to $E' = 8$

Load for first NOT gates connected to $s_i = 5$

Load for second NOT gates = 4

Load for AND gates = 1

Load for OR gate = $L1 + 1$

where $L1$ is load on output z

Load for last NOT gate = L_2
 where L_2 is the Load on the output z'
 For delay:

$$AND(x_4, x_3, x_2, x_1, x_0) = AND(AND(x_4, x_3, x_2), AND(x_1, x_0))$$

and

$$OR(x_7, x_6, \dots, x_1, x_0) = OR(OR(x_7, x_6, x_5, x_4), OR(x_3, x_2, x_1, x_0))$$

Let :

$$t_{pLH}(AND-5) = T_1$$

$$t_{pHL}(AND-5) = T_2$$

$$t_{pLH}(OR-8) = T_3$$

$$t_{pHL}(OR-8) = T_4$$

Then :

$$T_1 = t_{pLH}(AND-3) + t_{pLH}(AND-2) = 0.2 + 0.038 + 0.15 + 0.037 = 0.43$$

$$T_2 = t_{pHL}(AND-3) + t_{pHL}(AND-2) = 0.18 + 0.018 + 0.16 + 0.017 = 0.38$$

$$T_3 = t_{pLH}(OR-4) + t_{pLH}(OR-2) = 0.13 + 0.038 + 0.12 + 0.037(L_1 + 1) = 0.33 + 0.037L_1$$

$$T_4 = t_{pHL}(OR-4) + t_{pHL}(OR-2) = 0.45 + 0.025 + 0.2 + 0.019(L_1 + 1) = 0.69 + 0.019L_1$$

The critical path delay is:

$$\begin{aligned} t_{pLH}(s_2, z') &= t_{pLH}(NOT) + t_{pHL}(NOT) + t_{pHL}(AND-5) + t_{pHL}(OR-8) + t_{pLH}(NOT) \\ &= 0.02 + 0.038 \times 5 + 0.05 + 0.017 \times 4 + T_2 + T_4 + 0.02 + 0.038 \times L_2 \\ &= 0.35 + T_2 + T_4 + 0.038 \times L_2 \end{aligned}$$

$$\begin{aligned} t_{pHL}(s_2, z') &= t_{pHL}(NOT) + t_{pLH}(NOT) + t_{pLH}(AND-5) + t_{pLH}(OR-8) + t_{pHL}(NOT) \\ &= 0.05 + 0.017 \times 5 + 0.02 + 0.038 \times 4 + T_1 + T_3 + 0.05 + 0.017 \times L_2 \\ &= 0.36 + T_1 + T_3 + 0.017 \times L_2 \end{aligned}$$

d.

