## CS M51A, Sec. 1, Class Exercises No. 7

Exercise 7.15 Determine the minimal state table that is equivalent to the following

PS	Input	
	x = 0	x = 1
a	f, 0	b, 0
b	d, 0	c, 0
c	f, 0	e, 0
d	g, 1	a, 0
e	d, 0	c, 0
f	f, 1	b, 1
g	g, 0	h, 1
h	g, 1	a, 0
	NS, z	